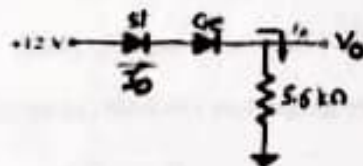


Time 3 Hours



Note: Attempt any two part from each question.

Max. Marks: 60


- Q.1 (a) Write down difference between following. (6)
- n-type and p-type semiconductor materials.
 - donor and acceptor impurities.
 - majority and minority carriers.
- (b) Determine V_o and I_D for the given circuit. (6)



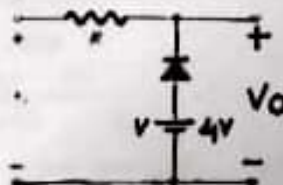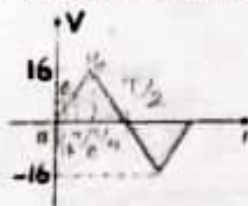
- (c) Draw the V-I characteristics of Silicon diode, Zener diode, LED, Photo diode and ideal diode. (6)
- Q.2 (a) Determine V_o for the given network. (6)



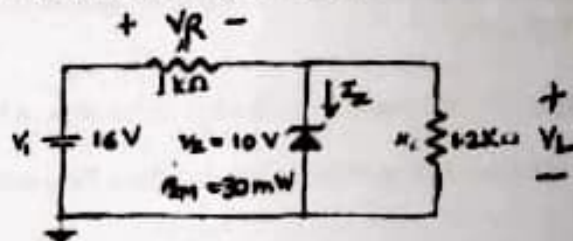- (b) Determine V_L , V_R , I_Z , and P_Z for given circuit. (6)



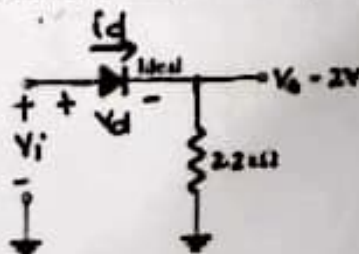- (c) Assuming an ideal diode, sketch v_i , v_d , and i_d for the half-wave rectifier of Fig. The input is a sinusoidal waveform with a frequency of 60 Hz. Repeat, Problem with a silicon diode ($V_T = 0.7$ V). (6)



2023020


BE 1 year Computer Engineering B
 Subject Name:- Basic Electronics
 Subject Code:- 1ETRC4

Time: 3 hours


Max Marks:60

Note:- All question carry equal marks. Attempt any two part from each question

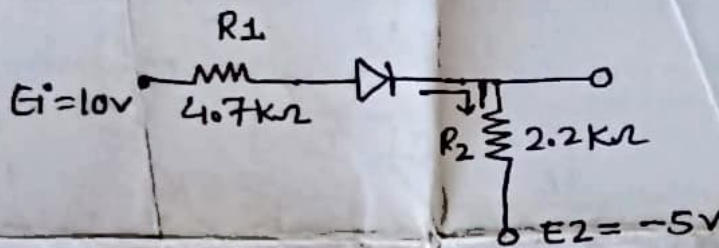- Q.1 a) Draw the ideal diode V-I characteristic and explain the working of the PN junction diode (6)
- b) Consider a pn junction at equilibrium at room temperature ($T=300K$) for which the doping concentrations are $N_a = 10^{12}/cm^3$ and $N_d = 10^{11}/cm^3$ and the cross-sectional area $A=10^{-2}cm^2$. Calculate p_p , n_{p0} , n_n , p_{n0} , V_0 , W , x_n , x_p and Q_j . Use $n_i=1.2 \times 10^9/cm^3$. (6)
- c) Derive the diode current equation and what parameters it depends on. (6)
- Q.2 a) Determine I_D , I_{R1} , I_{R2} , V_0 , V_{R1} and V_{R2} use practical diode model. (6)




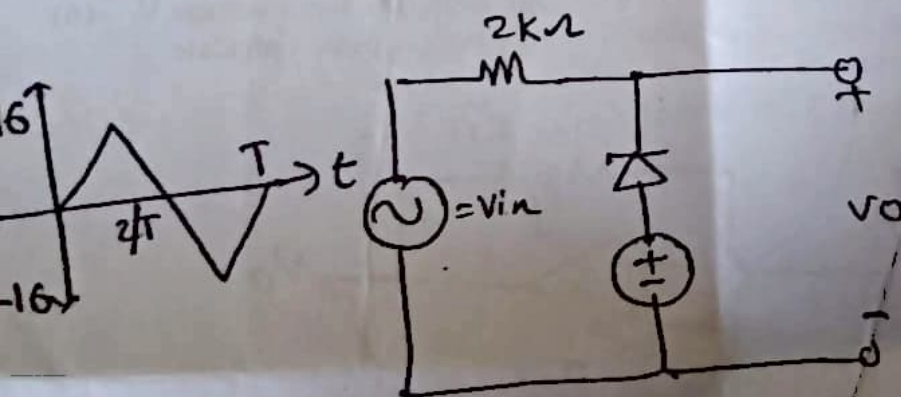- b) Determine the output v_o waveform for circuit below.



- c) Explain the working of a full wave bridge rectifier with the help of a circuit diagram. Also, draw output waveform

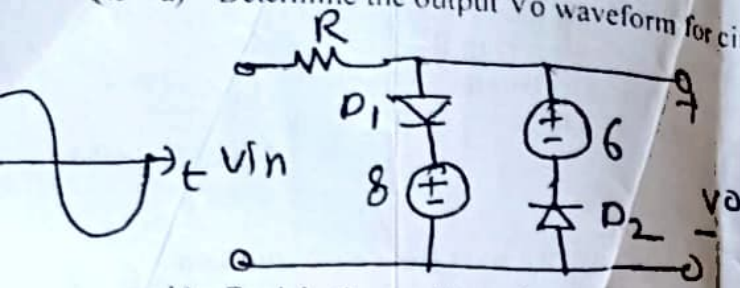Q.3 a) Determine the output V_o waveform for circuit below. (6)



b) Explain the working of a photodiode and Zener diodes. *Derive the ripple factor equation for Full wave rectifier.* (6)

c) Explain the working of Photodiode and Zener with the help of V-I characteristic (6)


Q.4 a) Draw the different configurations of the PNP transistor. Explain the following: (6)

(1) Why is the collector wider than the emitter and base?

(2) why is a transistor low-powered device?

b) Define dc alpha and ac alpha. A transistor has $I_B = 105\mu A$ and $I_C = 2.05mA$. find (1) β , (2) α , (3) I_E (6)

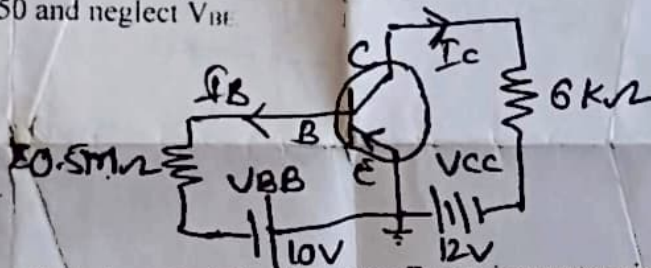c) For the circuit shown in fig. draw the dc load line and locate the dc working point. Assume $\beta = 50$ and neglect V_{BE} . (6)




Q.5 a) Write the practical characteristic of op-amp. For an integrator circuit $V_1(t) = 1 \sin \omega t$. If $R_1 = 4K\Omega$ and $C = 2\mu F$. find V_0 at $\omega t = \pi/2$, if $V_0(0) = 0$ and $\omega = 1MHz$. (6)

b) A non-inverting amplifier is shown in fig. the loop gain $A = 50,000$. Input voltage $V_i = 0.5V$ average d.c with a.c sine wave component of $0.3V$ peak to peak. Calculate (6)

(i) closed loop gain assuming $A = \text{Infinite}$ and

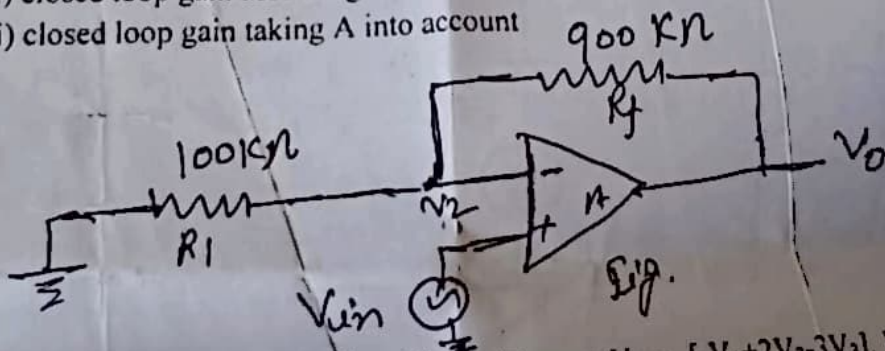(ii) closed loop gain taking A into account



c) Sketch the circuit of summer using OP-AMP to get $V_o = -[V_1 + 2V_2 + 3V_3]$. Explain the virtual ground concept in an OP-AMP. (6)