


Time 3 Hours

Max. Marks: 60

Note: Attempt any two part from each question.



- Q.1 (a) Write down difference between following. (6)
- n-type and p-type semiconductor materials.
  - donor and acceptor impurities.
  - majority and minority carriers.

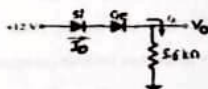- (b) Determine  $V_o$  and  $I_D$  for the given circuit. (6)




- (c) Draw the V-I characteristics of Silicon diode, Zener diode, LED, Photo diode and ideal diode. (6)

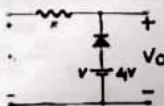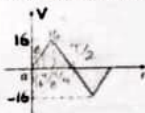
- Q.2 (a) Determine  $V_o$  for the given network. (6)



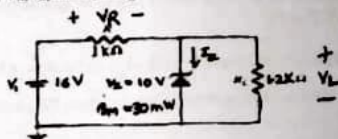- (b) Determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$  for given circuit. (6)



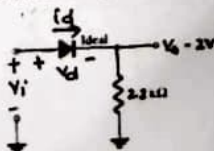
- (c) Assuming an ideal diode, sketch  $v_i$ ,  $v_d$ , and  $i_d$  for the half-wave rectifier of Fig. The input is a sinusoidal waveform with a frequency of 60 Hz. Repeat, Problem with a silicon diode ( $V_T = 0.7$  V). (6)



7021239

- Q.3 (a) I. Sketch Output characteristic of BJT in Common Base configuration. What kind of information does it reveals? (6)
- Derive expressions for Stability Factors  $S$ ,  $S'$  and  $S''$  for BJT in Collector to Base bias configuration.

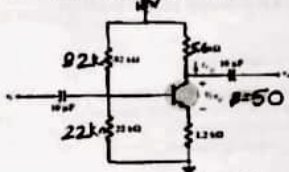- (b) I. Determine Q- point for the circuit below: (6)




- II. Classify and State different types of Amplifiers.

- (c) Explain working of BJT Differential Amplifier circuit. (6)

- Q.4 (a) Explain with necessary circuits how OP-AMP can be used to filter different frequency signals (6)

- (b) It is require to implement the function  $C = 4 * (A - B)$  in hardware, where A and B are two voltage sources and C is the output voltage. Draw and explain the circuit to meet the same. (6)

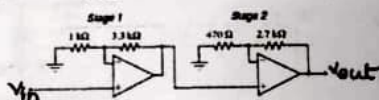- (c) Calculate the voltage gain for each stage of this amplifier circuit, then calculate the overall voltage gain: (6)



- Q.5 (a) Sketch and explain re model for BJT in CE configuration. State relation between  $\alpha$ ,  $\beta$  and  $\gamma$ . (6)

- (b) Compare positive and negative feedback with the help of block diagram. (6)

- (c) State the purpose of using Schmitt Trigger. Draw the circuit and Explain the same. (6)

2023020


BE 1 year Computer Engineering B  
 Subject Name:- Basic Electronics  
 Subject Code:- 1ETRC4

Time: 3 hours


Max Marks:60

Note:- All question carry equal marks. Attempt any two part from each question

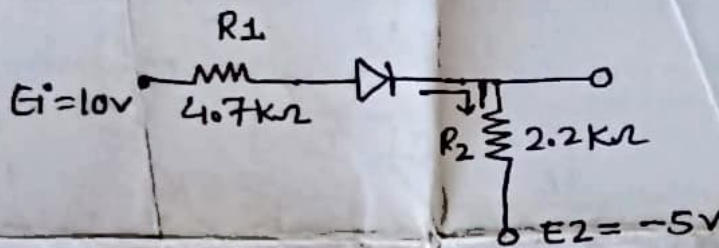- Q.1 a) Draw the ideal diode V-I characteristic and explain the working of the PN junction diode (6)
- b) Consider a pn junction at equilibrium at room temperature ( $T=300K$ ) for which the doping concentrations are  $N_a = 10^{12}/cm^3$  and  $N_d = 10^{11}/cm^3$  and the cross-sectional area  $A=10^{-2}cm^2$ . Calculate  $p_p$ ,  $n_{p0}$ ,  $n_n$ ,  $p_{n0}$ ,  $V_0$ ,  $W$ ,  $x_n$ ,  $x_p$  and  $Q_j$ . Use  $n_i=1.2 \times 10^9/cm^3$ . (6)
- c) Derive the diode current equation and what parameters it depends on. (6)
- Q.2 a) Determine  $I_D$ ,  $I_{R1}$ ,  $I_{R2}$ ,  $V_0$ ,  $V_{R1}$  and  $V_{R2}$  use practical diode model. (6)



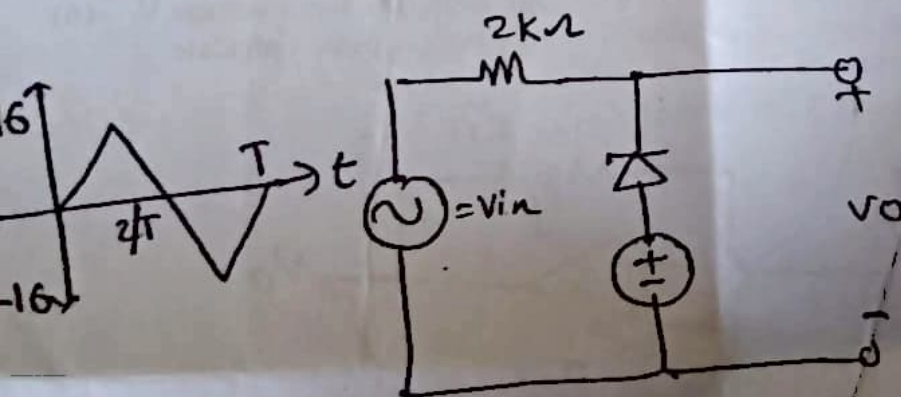
- b) Determine the output  $v_o$  waveform for circuit below.



- c) Explain the working of a full wave bridge rectifier with the help of a circuit diagram. Also, draw output waveform



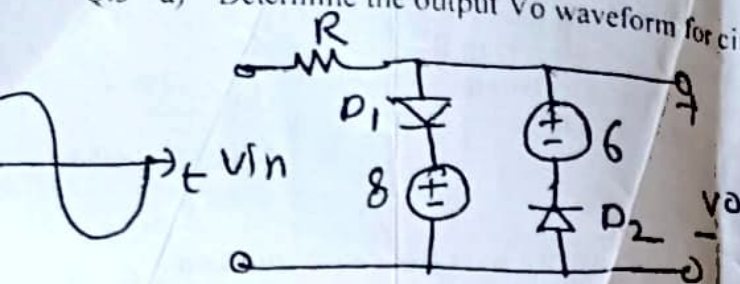Q.3 a) Determine the output  $V_o$  waveform for circuit below. (6)



b) Explain the working of a photodiode and Zener diodes. *Derive the ripple factor equation for full wave rectifier.* (6)

c) Explain the working of Photodiode and Zener with the help of V-I characteristic (6)


Q.4 a) Draw the different configurations of the PNP transistor. Explain the following: (6)

(1) Why is the collector wider than the emitter and base?

(2) why is a transistor low-powered device?

b) Define dc alpha and ac alpha. A transistor has  $I_B = 105\mu A$  and  $I_C = 2.05mA$ . find (1)  $\beta$ , (2)  $\alpha$ , (3)  $I_E$  (6)

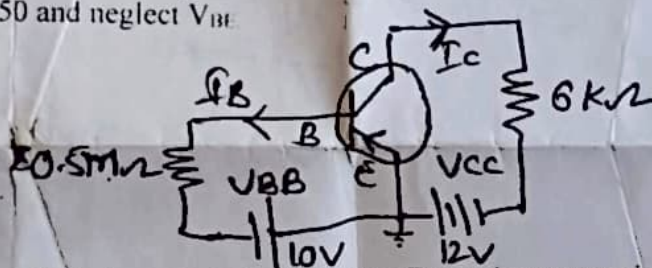c) For the circuit shown in fig. draw the dc load line and locate the dc working point. Assume  $\beta = 50$  and neglect  $V_{BE}$ . (6)




Q.5 a) Write the practical characteristic of op-amp. For an integrator circuit  $V_1(t) = 1 \sin \omega t$ . If  $R_1 = 4K\Omega$  and  $C = 2\mu F$ . find  $V_0$  at  $\omega t = \pi/2$ , if  $V_0(0) = 0$  and  $\omega = 1MHz$ . (6)

b) A non-inverting amplifier is shown in fig. the loop gain  $A = 50,000$ . Input voltage  $V_i = 0.5V$  average d.c with a.c sine wave component of  $0.3V$  peak to peak. Calculate (6)

(i) closed loop gain assuming  $A = \text{Infinite}$  and

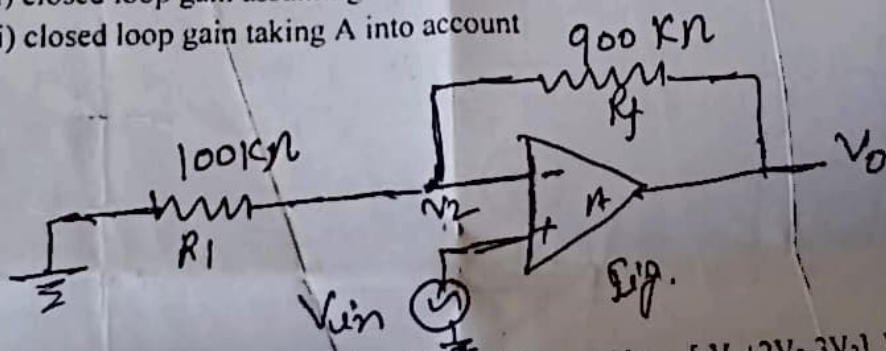(ii) closed loop gain taking  $A$  into account



c) Sketch the circuit of summer using OP-AMP to get  $V_o = -[V_1 + 2V_2 + 3V_3]$ . Explain the virtual ground concept in an OP-AMP. (6)